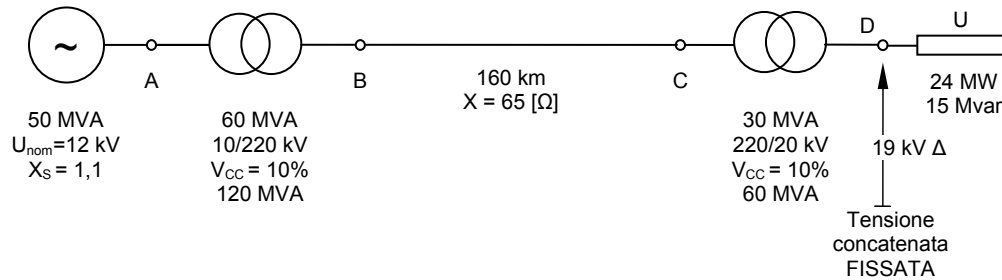


# ESEMPIO METODO P.U. Esercizio Numero 2 PAG. 135 libro del prof. Antonio Paolucci



GENERATORE	TRAFO1	LINEA	TRAFO2 CARICO
$X_s = \frac{1,1 \cdot 12000^2}{50 \cdot 10^6} = 3,168 \text{ [}\Omega\text{]}$	$X_{T1} = \frac{0,1 \cdot 20000^2}{60 \cdot 10^6} = 0,667 \text{ [}\Omega\text{]}$	$X_L = 65 \cdot \left(\frac{20}{220}\right)^2 = 0,53719 \text{ [}\Omega\text{]}$	$X_{T2} = \frac{0,1 \cdot 20000^2}{30 \cdot 10^6} = 1,33 \text{ [}\Omega\text{]}$
$X_s = \frac{3,168}{\left(\frac{10}{20}\right)^2} = 12,672 \text{ [}\Omega\text{]}$ Impedenza riferita a 20 kV			$r = \frac{19000^2}{26 \cdot 10^6} = 15,042 \text{ [}\Omega\text{]}$
			$x = \frac{19000^2}{15 \cdot 10^6} = 24,066 \text{ [}\Omega\text{]}$

$$Z_{TOT} = jX_S + jX_{T1} + jX_L + jX_{T2} = jX_{TOT} = j15,21 \text{ [}\Omega\text{]}$$

$$I_{caricoA} = \frac{24 \cdot 10^6}{\sqrt{3} \cdot 19000} = 729 \text{ [A]}$$

$$I_{caricoR} = \frac{15 \cdot 10^6}{\sqrt{3} \cdot 19000} = 455,8 \text{ [A]}$$

Tensione interna di macchina (riferita a 20 kV)

$$E_S = E_D + jX_{TOT} \cdot I_{CAR}$$

$$E_{S\_20kV} = \frac{19000}{\sqrt{3}} + j15,21 \cdot (729 - j455,8) = 17,90 + j11,088 \text{ [kV]}$$

$$E_{S\_10kV} = \frac{17,90 + j11,088}{2} = 8,95 + j5,544 \text{ [kV]}$$

E in corto circuito in D? (mantenendo la tensione a 19 kV concatenati)

$$Z_{eq} = \frac{1}{\left(\frac{1}{r}\right) + \left(\frac{1}{jX_{carico}}\right) + \left(\frac{1}{jX_{tot}}\right)} = 4,17 - j6,73 [\Omega]$$

$$I_{cc3f} = \frac{19000}{\sqrt{3} \cdot (4,13 + j6,83)} = 729 - j1177 [A]$$

E in p.u. cosa succede?

$N_{base}(\text{trifase}) = 60 \text{ MVA}$

$E_{base1} = \frac{10000}{\sqrt{3}}$	$E_{base2} = \frac{220000}{\sqrt{3}}$	$E_{base3} = \frac{20000}{\sqrt{3}}$
$I_{base1} = \frac{N_{base}}{3E_{base1}} = 3464 \text{ A}$	$I_{base2} = \frac{N_{base}}{3E_{base2}} = 157,45 \text{ A}$	$I_{base3} = \frac{N_{base}}{3E_{base3}} = 1,73 \text{ kA}$
$Z_{base1} = \frac{E_{base1}}{I_{base1}} = 1,66 \Omega$	$Z_{base2} = \frac{E_{base2}}{I_{base2}} = 806 \Omega$	$Z_{base3} = \frac{E_{base3}}{I_{base3}} = 6,66 \Omega$

$e_d = \frac{E_D}{E_{base3}} = \frac{19000/\sqrt{3}}{E_{base3}} = 0,95 \text{ p.u.}$	$x_L = \frac{65}{806} = 0,081 \text{ p.u.}$
$x_s = \frac{X_S}{Z_{base1}} = \frac{3,168}{1,66} = 1,91 \text{ p.u.}$	$x_{tot} = 2,229 \text{ p.u.}$
$x_{T1} = \frac{0,1 \cdot 220000^2}{60 \cdot 10^6} \cdot \frac{1}{806} = 0,1 \text{ p.u.}$	$n_d = \frac{24 + j15}{60} = 0,4 + j0,25 \text{ p.u.}$
$x_{T2} = \frac{1,33}{6,66} = 0,2 \text{ p.u.}$	$n_d = e_d \cdot \check{i}_d \Rightarrow \check{i}_d = \frac{\check{n}_d}{e_d} = \frac{0,4 - j0,25}{0,95} = 0,42 - j0,263 \text{ p.u.}$

$r = \frac{e_d^2}{p} = \frac{0,95^2}{0,4} = 2,25625 \text{ p.u.}$	$x = \frac{e_d^2}{q} = \frac{0,95^2}{0,25} = 3,61 \text{ p.u.}$
$e_s = e_d + jx_{tot} \cdot i_d = 0,95 + j2,29 \cdot (0,42 - j0,263) = 1,55 + j0,962 \text{ p.u.}$	
$E_s = e_s \cdot E_{base1} = (1,55 + j0,962) \cdot \frac{10000}{\sqrt{3}} = (8,96 + j5,55) \text{ kV}$	

E in corto circuito in D? (mantenendo a 19 kV concatenati)

$$\underline{z}_{eq} = \frac{1}{\left(\frac{1}{r}\right) + \left(\frac{1}{jX_{carico}}\right) + \left(\frac{1}{jX_{tot}}\right)} = 0,627 + j1,01 \text{ p.u.}$$

$$i_{cc3f} = \frac{e_d}{\underline{z}_{eq}} = \frac{0,95}{0,627 + j1,01} = 0,421 - j0,678 \text{ p.u.}$$

$$I_{cc3f} = i_{cc3f} \cdot I_{base3} = 729 - j1174 \text{ [A]}$$