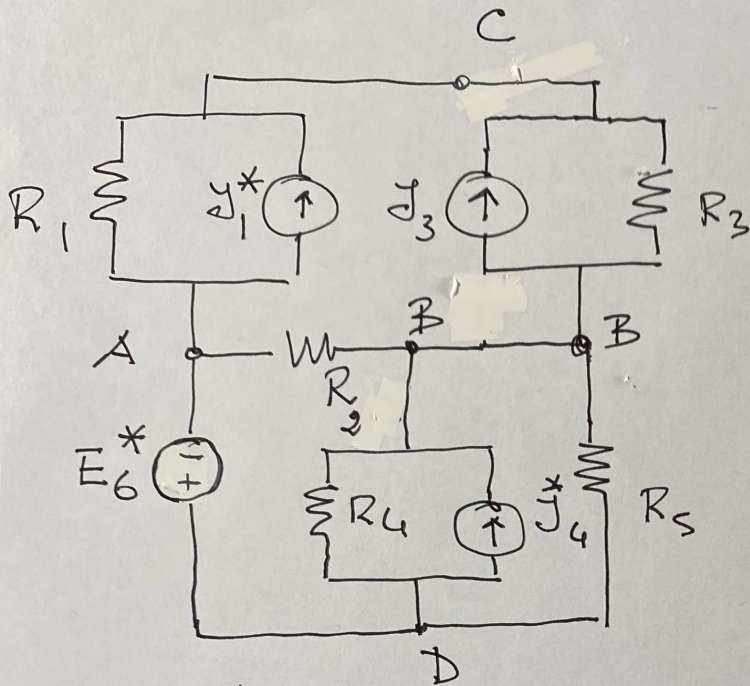



ESERCIZIO ASSEGNATO SABATO 28/03



$$J_1^* = E_1 / R_1$$

$$J_4^* = E_4 / R_4$$

$$R_{45} = \frac{R_4 R_5}{R_4 + R_5}$$

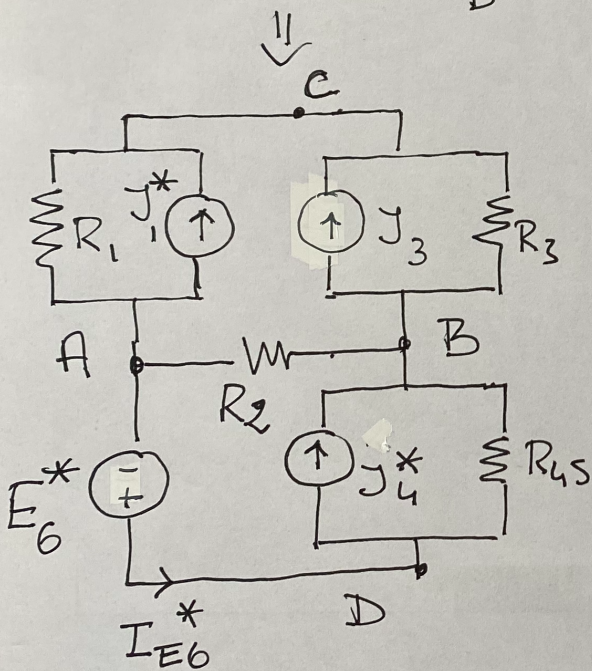

$$U_A = 0$$

$$B: \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_{45}} \right) U_B - \frac{1}{R_3} U_C - \frac{1}{R_{45}} U_D = -J_3 + J_4^*$$

$$C: -\frac{1}{R_3} U_B + \left(\frac{1}{R_1} + \frac{1}{R_3} \right) U_C - 0 \cdot U_D = J_1^* + J_3$$

$$D: -\frac{1}{R_{45}} U_B - 0 \cdot U_C + \frac{1}{R_{45}} U_D = -J_4^* - I_{E6}^*$$

$$X: U_D = E_6^*$$

$$\Rightarrow U_B = 40 \text{ V} \quad U_C = -20 \quad U_D = 70 \quad \text{N.B.: BeC sistema } 2 \times 2$$

$$I_{E6}^* = 40$$

Poi: $V_{CA} = U_C = E_1 - R_1 I_{E1} \Rightarrow I_{E1} = (E_1 - U_C) / R_1 = -38$

$$I_{E6} = I_{E6}^* + \frac{E_6}{R_6} = 81$$

RETE ORIGINALI